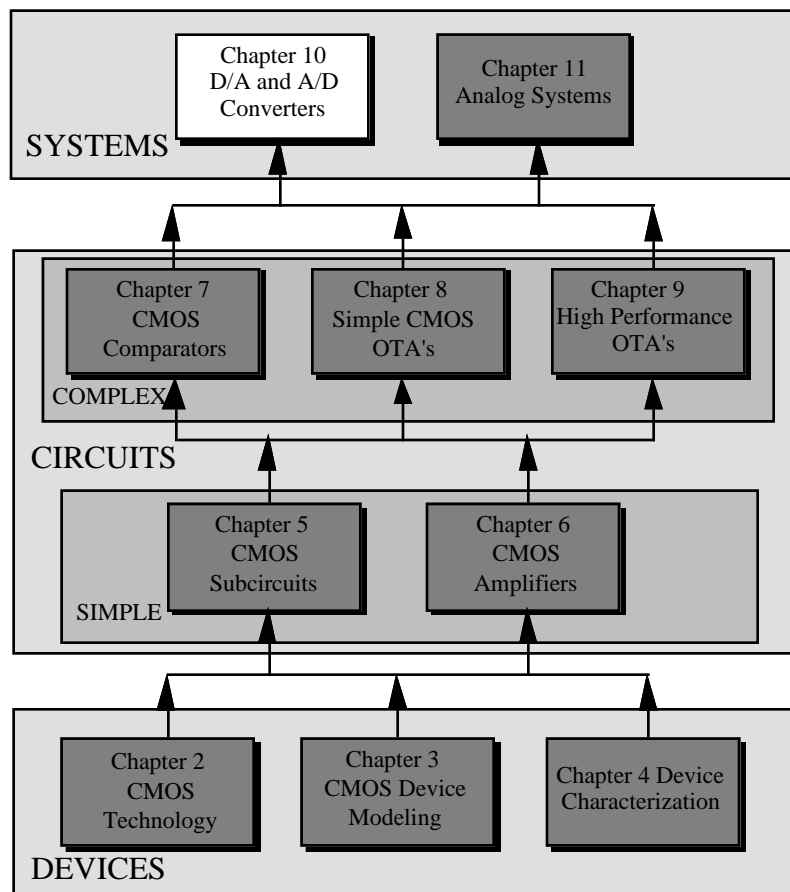


## X. CMOS DATA CONVERTERS


### Contents

- X.1 Characterization and definition of D/A converters
- X.2 Voltage scaling D/A converters
- X.3 Charge scaling D/A converters
- X.4 Voltage and charge scaling D/A converters
- X.5 Other types of D/A converters,
- X.6 Characterization and definition of A/D converters
- X.7 Serial A/D converters
- X.8 Medium-speed A/D converters
- X.9 High-speed A/D converters (Flash, two-step, multiple pipe)
- X.10 Oversampled A/D converters
- X.11 Examples of A/D converters, limits of A/D converters

 
### Organization



Importance of Data Converters in Signal Processing




A/D and D/A Converters in Data Systems

 

## X.1 - CHARACTERIZATION AND DEFINITION OF CONVERTERS
 
### General Concept of Digital-to-Analog (D/A) Converters



$$v_{OUT} = KV_{ref}D \quad \text{or} \quad i_{OUT} = KI_{ref}D$$

where

$K$  = gain constant (independent of digital input)

$$D = \frac{b_0}{2^N} + \frac{b_1}{2^{N-1}} + \frac{b_2}{2^{N-2}} + \dots + \frac{b_{N-1}}{2^1} = \text{scaling factor}$$

$V_{ref}$  ( $I_{ref}$ ) = voltage (current) reference

$b_{N-1}$  = most significant bit (MSB)


$b_0$  = least significant bit (LSB)

For example,


$$\begin{aligned} v_{OUT} &= KV_{ref} \left( \frac{b_0}{2^N} + \frac{b_1}{2^{N-1}} + \frac{b_2}{2^{N-2}} + \dots + \frac{b_{N-1}}{2^1} \right) \\ &= KV_{ref} \frac{1}{2^N} \sum_{j=0}^{N-1} b_j 2^j \end{aligned}$$

Basic Architecture of a D/A Converter

Continuous Time D/A Converter-

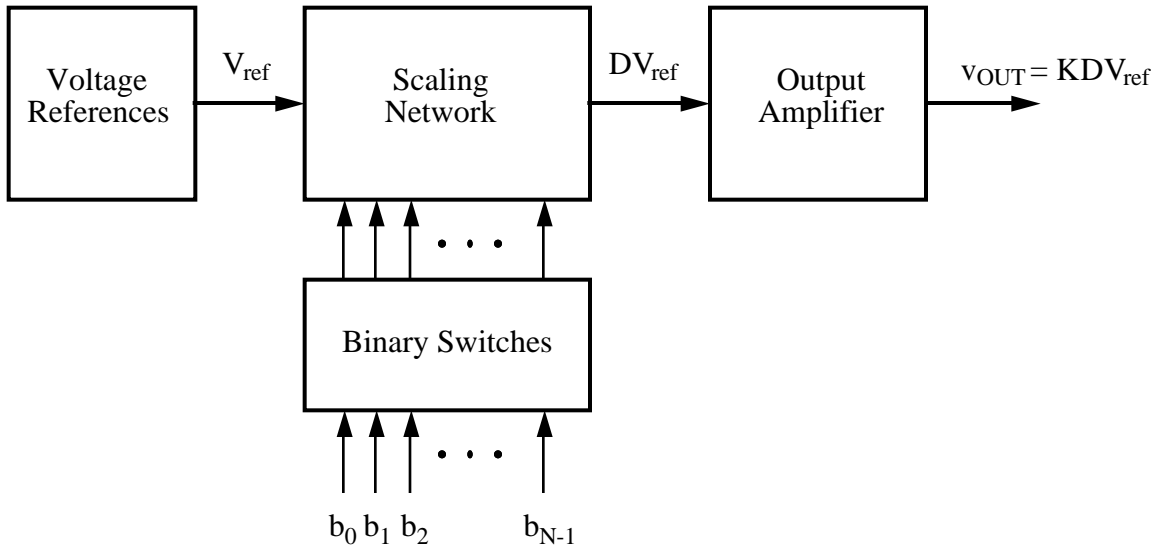


Clocked D/A Converter-

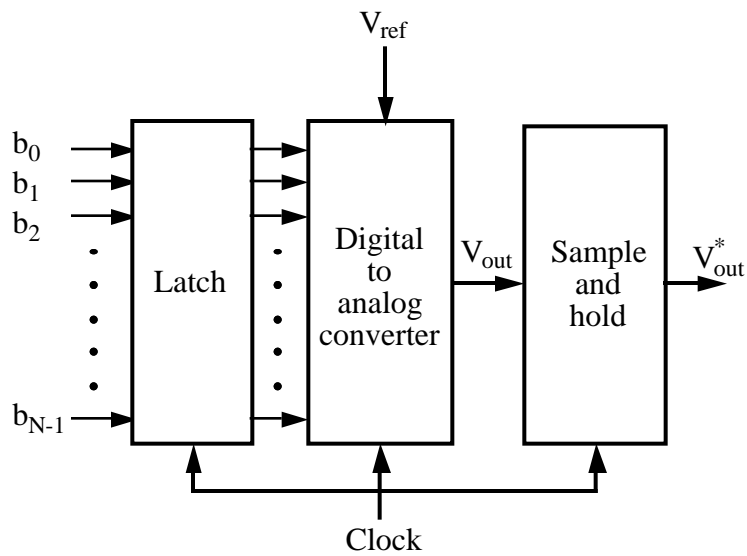


Classification of D/A Converters

Done by how the converter is scaled-

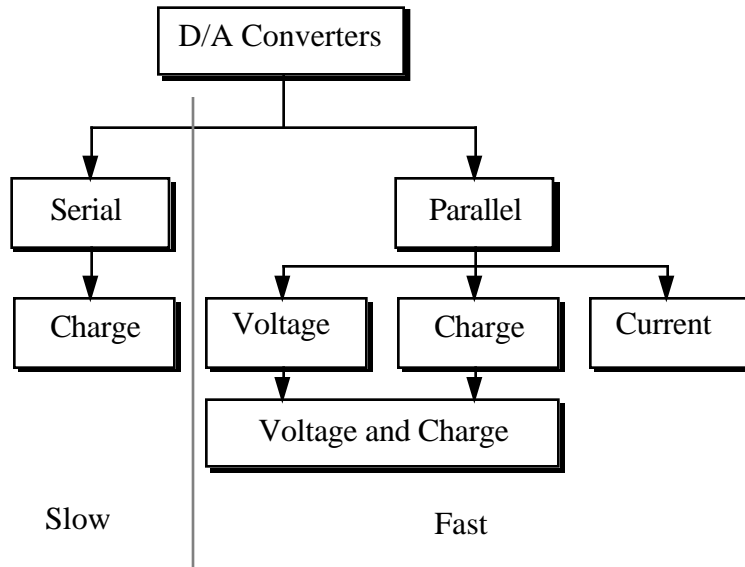

Static Characterization of D/A Converters

 Ideal input-output D/A converter Static Characteristic -




An ideal LSB change causes an analog change of  $\frac{V_{\text{ref}}}{2^N}$
 
## Definitions

*Resolution* is the smallest analog change resulting from a 1 LSB digital change (quantified in terms of N bits).

*Quantization Noise* is the inherent uncertainty in digitizing an analog value with a finite resolution converter.



*Dynamic range (DR)* is the ratio of FS to the smallest resolvable difference.

$$\text{DR} = \frac{\text{FS}}{\text{LSB change}} = \frac{V_{\text{REF}} \frac{2^N - 1}{2^N}}{V_{\text{REF}} \frac{1}{2^N}} = 2^N - 1$$

$$\text{DR(dB)} = 20 \log_{10}(2^N - 1) \cong 6N \text{ dB}$$

Signal to noise ratio (SNR) for a sawtooth waveform  
Approximating  $\text{FS} = \text{LSB}(2^N - 1) \cong \text{LSB}(2^N)$ ,

$$\text{SNR} = \frac{\text{Full scale RMS value}}{\text{RMS value of quantization noise}} = \frac{\frac{2^N}{2\sqrt{2}}}{\frac{1}{\sqrt{12}}} = \frac{\sqrt{12}}{2\sqrt{2}} 2^N$$

$$\text{SNR (dB)} = 20 \log_{10} \left[ \left( \frac{\sqrt{6}}{2} \right) 2^N \right] = 20 \log_{10} \left( \frac{\sqrt{6}}{2} \right) + 20 \log_{10}(2^N)$$

$$= 20 \log_{10}(1.225) + 6.02N = 1.76 \text{ dB} + 6.02N \text{ dB}$$



Definitions - Continued

*Full scale (FS)* is the the maximum DAC analog output value. It is one LSB less than  $V_{REF}$  .

$$FS = V_{REF} \frac{2^N - 1}{2^N}$$

A *monotonic* D/A (A/D) converter is one in which an increasing digital input code (analog input) produces a continuously increasing analog output value (digital output code).


*Offset error* is a constant shift of the actual finite resolution characteristic from the ideal infinite resolution characteristic.

*Gain error* is a deviation between the actual finite resolution characteristic and the ideal infinite resolution characteristic which changes with the input.

*Integral nonlinearity (INL)* is the maximum difference between the actual finite resolution characteristic and the infinite resolution characteristic.


*Differential nonlinearity (DNL)* is the maximum deviation of any analog output changes caused by an input LSB change from its ideal change of  $\frac{FS}{2^N}$ .

3-BIT D/A CONVERTER ILLUSTRATION

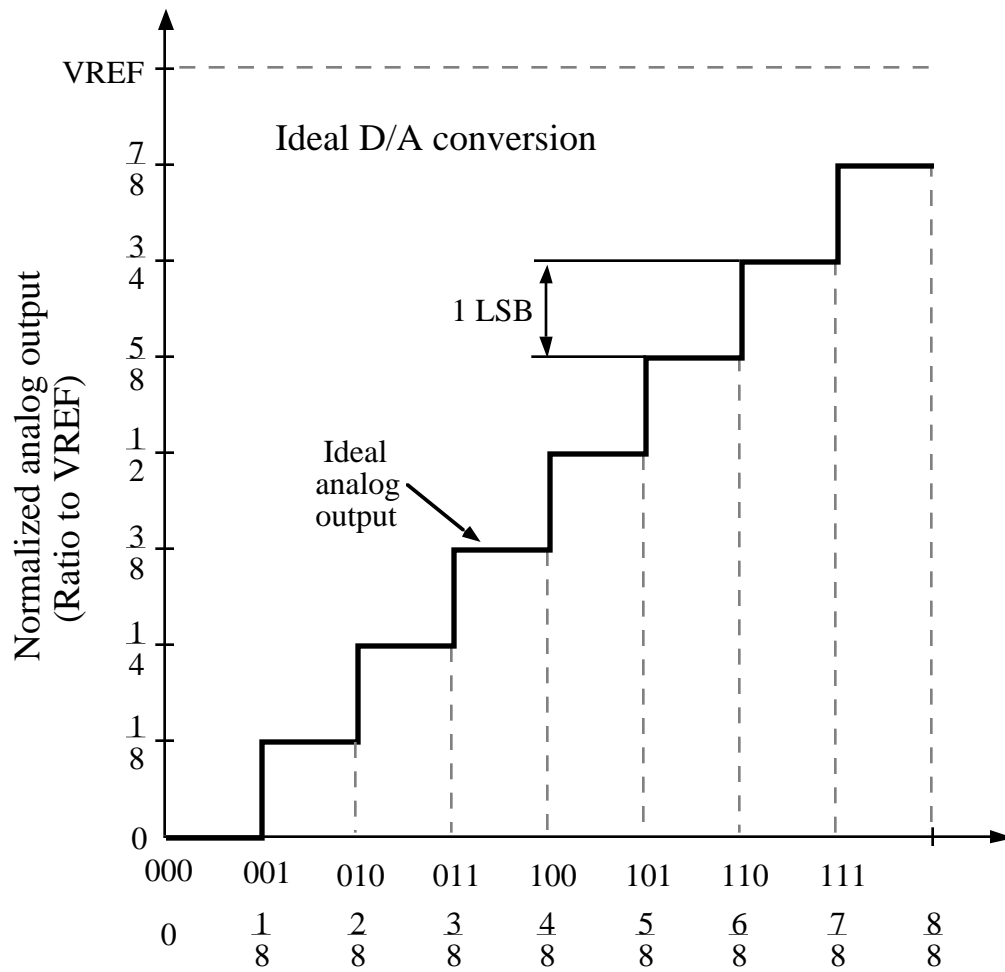

Digital input, code and fractional value


Ideal relationship

 


Typical sources of errors

Integral and Differential Linearity for a D/A Converter

 D/A Converter with  $\pm 1.5$  LSB integral nonlinearity and  $\pm 0.5$  LSB differential nonlinearity



 D/A converter with  $\pm 1$  LSB integral nonlinearity and  $\pm 1$  LSB differential nonlinearity




**X.2 VOLTAGE SCALING CONVERTERS****3-BIT VOLTAGE SCALING D/A CONVERTER**

Assume that  $b_0 = 1$ ,  $b_1 = 0$ , and  $b_2 = 1$

MSB:  $b_2$


LSB:  $b_0$

 

$$v_{\text{OUT}} = \frac{V_{\text{REF}}}{8} (D+0.5) = \frac{V_{\text{REF}}}{16} (2D+1) = 0.6875V_{\text{REF}} = \frac{11}{16} V_{\text{REF}}$$

### 3-BIT VOLTAGE SCALING D/A CONVERTER - CONT'D

Input-Output Characteristics:

 

Advantages:

- Inherent monotonicity

- Compatible with CMOS technology

- Small area if  $n < 8$  bits

Disadvantages:


- Large area if  $n > 8$  bits

- Requires a high input impedance buffer at output

- Integral linearity depends on the resistor ratios

3-BIT VOLTAGE SCALING D/A CONVERTER WHICH MINIMIZES THE SWITCHES

Require time for the logic to perform

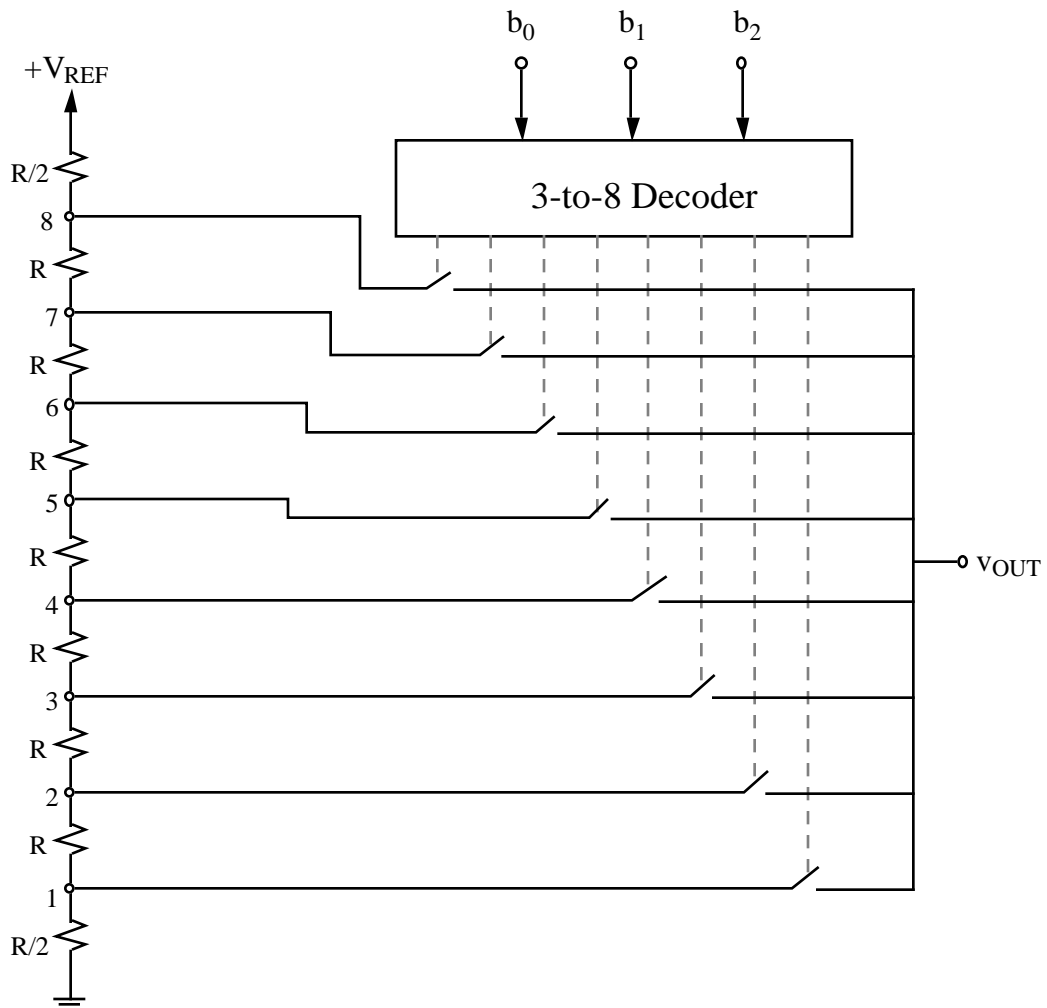

### Accuracy Requirements of a Voltage Scaling D/A

Find the accuracy requirements for the voltage scaling D/A converter as a function of the number of bits  $N$  if the resistor string is a 5 micron wide polysilicon strip. If the relative accuracy is 2%, what is the largest number of bits that can be resolved to within  $\pm 0.5$  LSB?

Assume that the ideal voltage to ground across  $k$  resistors is

$$V_k = \frac{kR}{2^N R} V_{REF}$$

The worst case variation in  $V_k$  is found by assuming all resistors above this point in the string are maximum and below this are minimum. Therefore,

$$V_k' = \frac{kR_{min} V_{REF}}{(2^N - k)R_{max} + kR_{min}}$$

The difference between the ideal and worst case voltages is,

$$\left| \frac{V_k}{V_{REF}} - \frac{V_k'}{V_{REF}} \right| = \left| \frac{kR}{2^N R} - \frac{kR_{min}}{(2^N - k)R_{max} + kR_{min}} \right|$$

Assuming that this difference should be less than 0.5 LSB gives,

$$\left| \frac{kR}{2^N R} - \frac{kR_{min}}{(2^N - k)R_{max} + kR_{min}} \right| < \frac{0.5}{2^N}$$

Expressing  $R_{max}$  as  $R + 0.5\Delta R$  and  $R_{min}$  as  $R - 0.5\Delta R$  and assuming the worst case occurs midway in the resistor string where  $k = 0.5(2^N)$  and assuming that 5 micron polysilicon has a 2% relative accuracy gives,


$$\left| 0.5 - \frac{0.5(R - 0.5\Delta R)}{0.5(R + 0.5\Delta R) + 0.5(R - 0.5\Delta R)} \right| = \left| \frac{1}{4} \frac{\Delta R}{R} \right| < \frac{1}{2} 2^{-N}$$

$$\Rightarrow \left| \frac{\Delta R}{R} \right| < \frac{1}{2^{N-1}} \quad \text{or} \quad |0.25(0.02)| < 0.5(2^{-N}) \Rightarrow N = 6$$




R-2R LADDER DAC's


Configuration:

 


Equivalent circuit at A:

 

Equivalent circuit at B:

 


Finally, the equivalent circuit at Q:

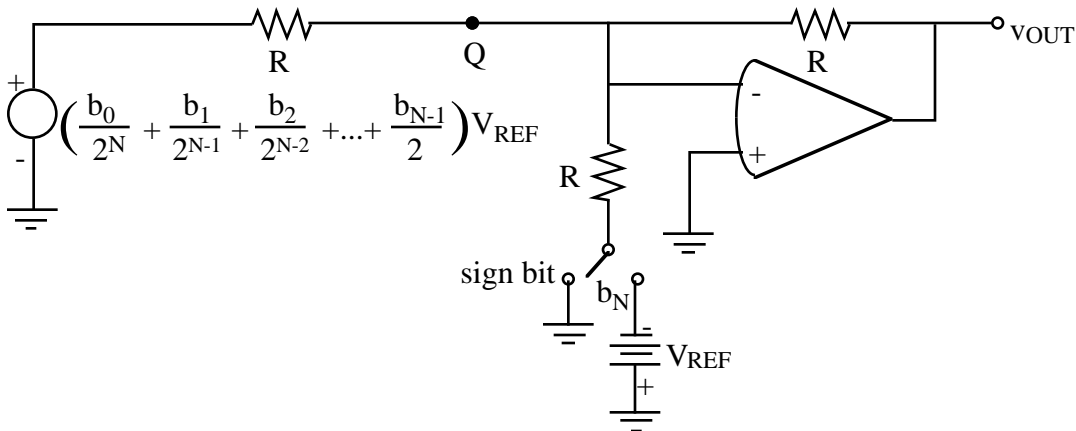

### X.3 CHARGE SCALING D/A CONVERTER

Binary weighted capacitor array:

 


Operation:

- 1.) During  $\phi_1$ , all capacitors are discharged.
- 2.) During  $\phi_2$ , capacitors with  $b_i = 1$  are connected to  $V_{REF}$  and capacitors with  $b_i = 0$  are grounded.
- 3.) The resulting output voltage is,

$$V_{OUT} = V_{REF} \left( \frac{b_{N-1}C}{2C} + \frac{b_{N-2}C/2}{2C} + \frac{b_{N-3}C/4}{2C} + \dots + \frac{b_0C/(2^{N-1})}{2C} \right)$$

If  $C_{eq.}$  is defined as the sum of all capacitances connected to  $V_{REF}$ , then
 
$$V_{OUT} = \left( \frac{C_{eq.}}{2C} \right) V_{REF}$$



### Other Versions of the Charge Scaling D/A Converter

#### Bipolar Operation:

Charge all capacitors to  $V_{REF}$ . If  $b_i = 1$ , connect the capacitor to ground, if  $b_i = 0$ , connect the capacitor to  $V_{REF}$ .

Will require an extra bit to decide whether to connect the capacitors initially to ground or to  $V_{REF}$ .

#### Four-Quadrant Operation:

If  $V_{REF}$  can have  $\pm$  values, then a full, four quadrant DAC can be obtained.

#### Multiplying DAC:

If  $V_{REF}$  is an analog signal (sampled and held), then the output is the product of a digital word and an analog signal and is called a multiplying DAC (MDAC).

### Influence of Capacitor Ratio Accuracy on No. of Bits

Use the data of Fig.2.4-2 to estimate the number of bits possible for a charge scaling D/A converter assuming a worst case approach and the worst conditions occur at the midscale (1 = MSB).

The ideal output of the charge scaling DA converter is,

$$\frac{V_{OUT}}{V_{REF}} = \frac{C_{eq.}}{2C}$$

The worst case output of the charge scaling DA converter is,

$$\frac{V'_{OUT}}{V_{REF}} = \frac{C_{eq.(min)}}{(2C - C_{eq.})_{(max)} + C_{eq.(min)}}$$

The difference between the ideal output and the worst case output is,

$$\left| \frac{V_{OUT}}{V_{REF}} - \frac{V'_{OUT}}{V_{REF}} \right| = \left| \frac{1}{2} - \frac{C_{eq.(min)}}{(2C - C_{eq.})_{(max)} \pm C_{eq.(min)}} \right|$$

Assuming the worst case condition occurs at midscale, then  $C_{eq.} = C$

$$\therefore \left| \frac{V_{OUT}}{V_{REF}} - \frac{V'_{OUT}}{V_{REF}} \right| = \left| \frac{1}{2} - \frac{C_{(min)}}{C_{(max)} - C_{(min)}} \right|$$

If  $C_{(max)} = C + 0.5\Delta C$  and  $C_{(min)} = C - 0.5\Delta C$ , then setting the difference between the ideal and worst case to 0.5LSB gives,

$$\frac{0.5(C_{(max)} \pm C_{(min)}) - C_{(min)}}{C_{(max)} + C_{(min)}} \leq 0.5(1/2^N)$$

or

$$C_{(max)} - C_{(min)} \leq \frac{1}{2^N} (C_{(max)} + C_{(min)})$$


or

$$\Delta C \leq \frac{1}{2^N} 2C \Rightarrow \left| \frac{\Delta C}{2C} \right| \leq 2^{-N} \Rightarrow \left| \frac{\Delta C}{C} \right| \leq \frac{1}{2^{N-1}}$$

A  $50\mu\text{m} \times 50\mu\text{m}$  unit capacitor gives a relative accuracy of 0.1% and  $N = 11$  bits. It is more appropriate that the relative accuracy is a function of  $N$ . For example, if  $\Delta C/C \approx 0.001 + 0.0001N$ , then  $N=9$  bits.


Increasing the Number of Bits for a Charge Scaling D/A Converter

 Use a capacitive divider. For example, a 13-bit DAC-



An equivalent circuit-
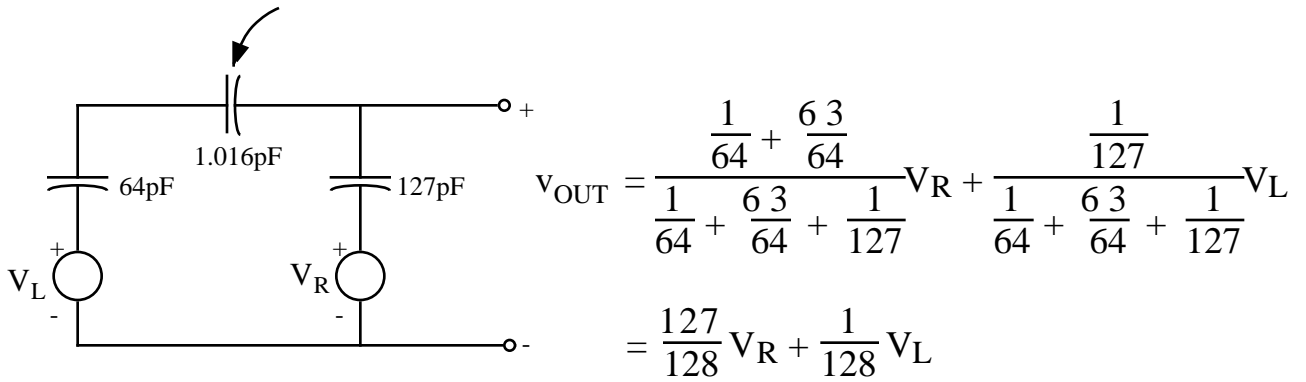
$$\frac{1}{64} + \frac{1}{C} = 1 \Rightarrow C = \frac{64}{63} \approx 1.016$$



$$V_R = \sum_{i=6}^{12} \frac{\pm b_i V_{REF} C_i}{127} \quad \text{and} \quad V_L = \sum_{i=0}^5 \frac{\pm b_i V_{REF} C_i}{64}$$


or

$$V_{OUT} = \frac{\pm V_{REF}}{128} \left[ \sum_{i=6}^{12} b_i C_i + \sum_{i=0}^5 \frac{b_i C_i}{64} \right]$$


### Removal of the Amplifier Input Capacitance Effects

Use the binary weighted capacitors as the input to a charge amplifier.

Example of A Two-Stage Configuration:

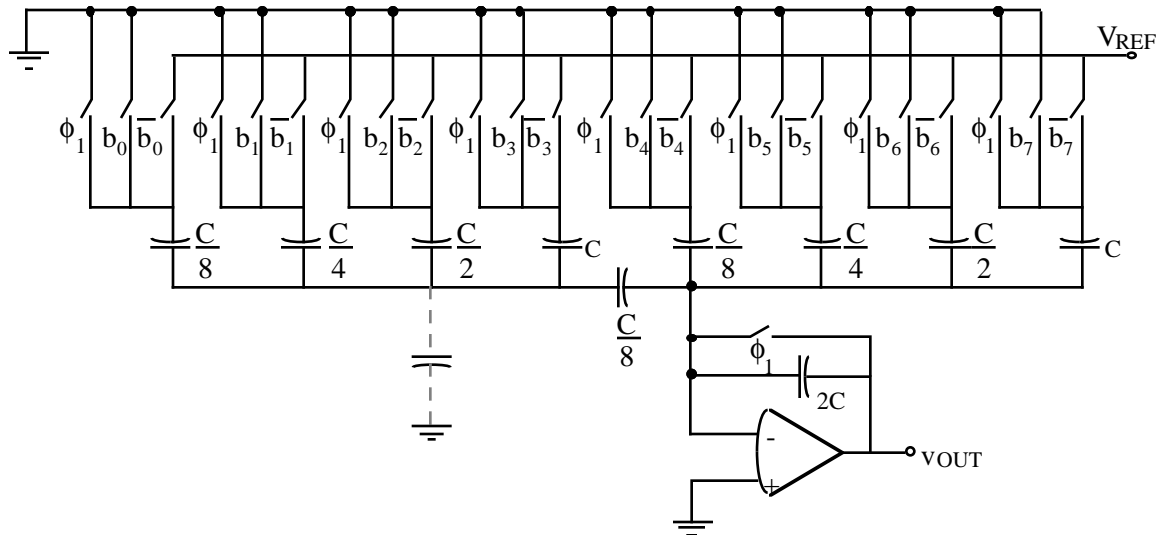
 
## X.4 - VOLTAGE SCALING-CHARGE SCALING DAC'S



Advantages:

- Resistor string is inherently monotonic so the first  $M$  bits are monotonic.
- Can remove voltage threshold offsets.
- Switching both busses A and B removes switch imperfections.
- Can make tradeoffs in performance between the resistors and capacitors.
- Example with 4 MSB's voltage scaling and 8 LSB's charge scaling:


Voltage Scaling, Charge Scaling DAC - Cont'd

Operation:


1.)  $S_F$ ,  $S_B$ , and  $S_{1B}$  through  $S_{k,B}$  are closed discharging all capacitors. If the output of the DAC is applied to any circuit having a nonzero threshold, switch  $S_B$  could be connected to this circuit to cancel this threshold effect.

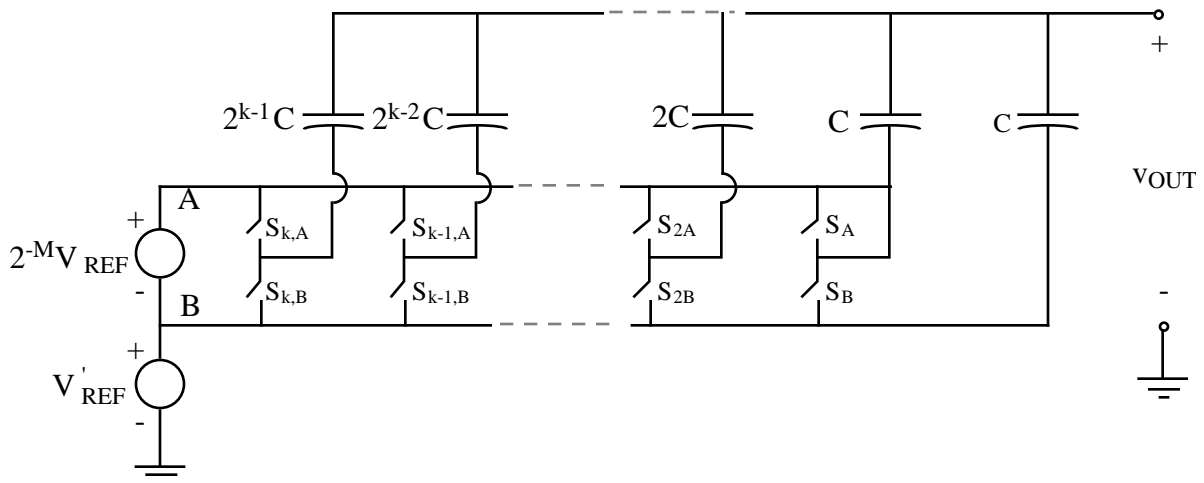2.) Switch  $S_F$  is opened and buses A and B are connected across the resistor whose lower and upper voltage is  $V'_{REF}$  and  $V'_{REF} + 2^{-M}V_{REF}$  respectively, where

$$V'_{REF} = V_{ref} \left( \frac{b_0}{2^M} + \frac{b_1}{2^{M-1}} + \frac{b_2}{2^{M-2}} + \dots + \frac{b_{M-1}}{2^1} \right)$$



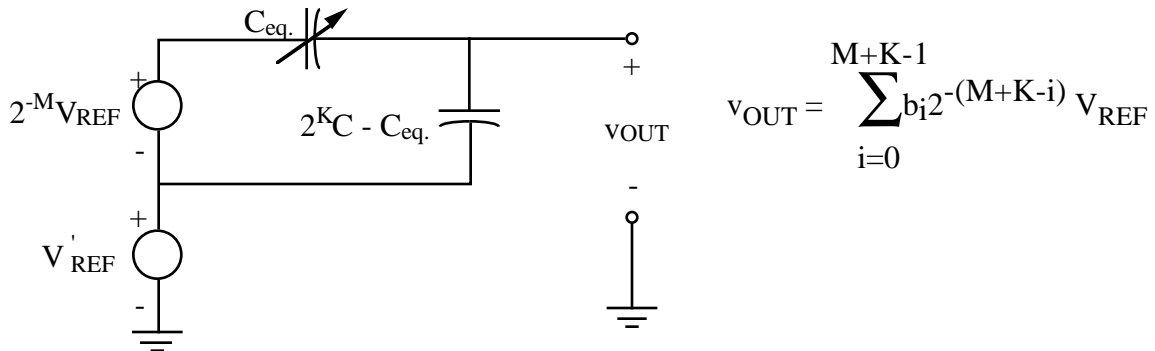
3.) Final step is to determine whether to connect the bottom plates of the capacitors to bus A ( $b_i=1$ ) or bus B ( $b_i=0$ ).




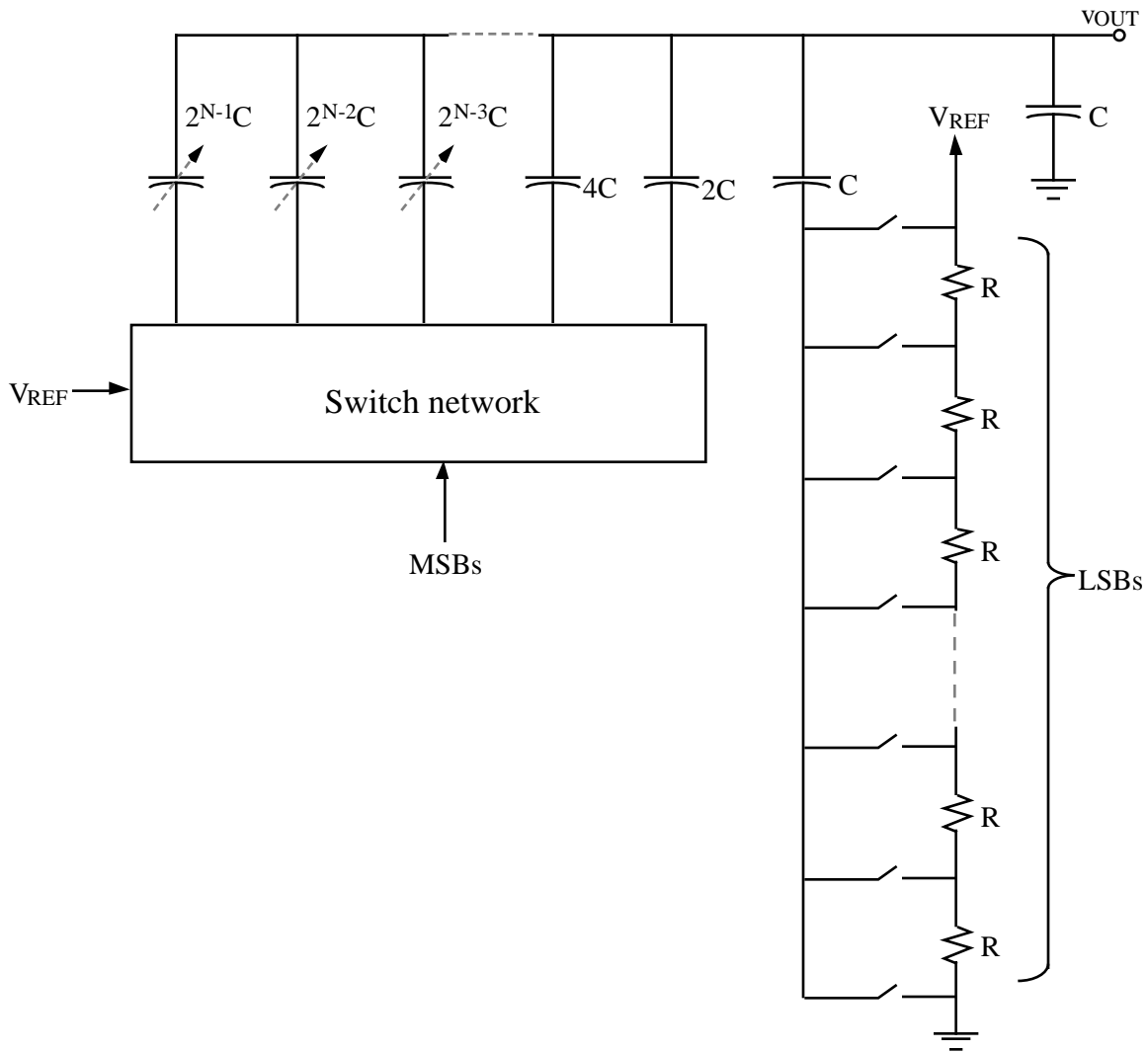
### Charge Scaling, Voltage Scaling DAC


Use capacitors for MSB's and resistors for LSB's



- Resistors must be trimmed for absolute accuracy.
- LSB's are monotonic.

### X.5- OTHER TYPES OF D/A CONVERTERS



#### CHARGE REDISTRIBUTION SERIAL DAC

 

Conversion sequence:

#### 4 Bit D/A Converter

INPUT WORD: 1101

  


- Close  $S_4$ :  $V_{C2} = 0$
- Start with LSB first-
- Close  $S_2$  ( $b_0=1$ ):  $V_{C1} = V_{REF}$
- Close  $S_1$ :  $V_{C1} = \frac{V_{REF}}{2} = V_{C2}$
- Close  $S_3$  ( $b_1=0$ ):  $V_{C1} = 0$
- Close  $S_1$ :  $V_{C1} = V_{C2} = \frac{V_{REF}}{4}$
- Close  $S_2$  ( $b_2=1$ ):  $V_{C1} = V_{REF}$
- Close  $S_1$ :  $V_{C1} = V_{C2} = \frac{5}{8} V_{REF}$
- Close  $S_2$  ( $b_3=1$ ):  $V_{C1} = V_{REF}$
- Close  $S_1$ :  $V_{C1} = V_{C2} = \frac{13}{16} V_{REF}$

Comments:

- LSB must go first.
- n cycles to make an n-bit D-A conversion.
- Top plate parasitics add error.
- Switch parasitics add error.

ALGORITHMIC SERIAL DAC

Pipeline Approach to Implementing a DAC:

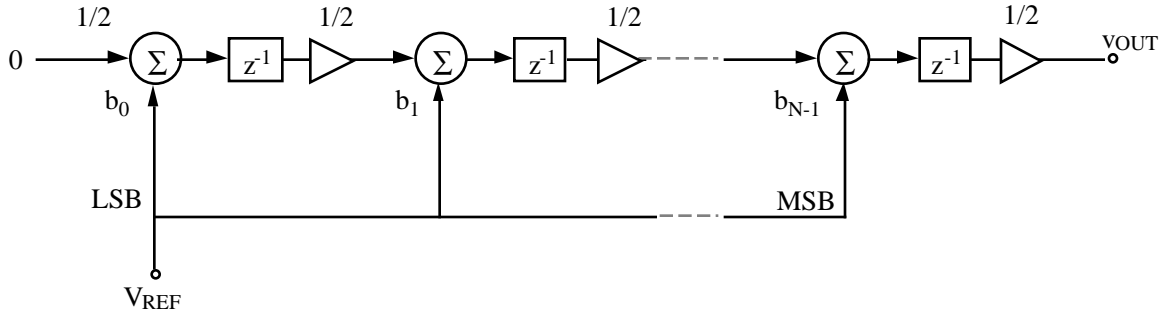

$$v_{\text{OUT}}(z) = \left[ \frac{b_{N-1}}{2} z^{-1} + \frac{b_{N-2}}{4} z^{-2} + \dots + \frac{b_0}{2^N} z^{-N} \right] V_{\text{REF}}$$

where  $b_i = 1$  or  $0$


Approaches:

- 1.) Pipeline with N cascaded stages.
- 2.) Algorithmic.

$$v_{\text{OUT}}(z) = \frac{b_i z^{-1} V_{\text{REF}}}{1 - 0.5z^{-1}}$$


### Example of an Algorithmic DAC Operation

Realization using iterative techniques:

 

Assume that the digital word is 11001 in the order of MSB to LSB. The steps in the conversion are:


- 1.)  $V_{OUT}(0)$  is zeroed.
- 2.) LSB = 1, switch A closed,  
 $V_{OUT}(1) = V_{REF}$ .
- 3.) Next LSB = 0, switch B closed,  
 $V_{OUT}(2) = 0 + 0.5V_{REF}$   
 $V_{OUT}(2) = 0.5V_{REF}$ .
- 4.) Next LSB = 0, switch B closed,  
 $V_{OUT}(3) = 0 + 0.25V_{REF}$   
 $V_{OUT}(3) = 0.25V_{REF}$ .
- 5.) Next LSB = 1, switch A closed,  
 $V_{OUT}(4) = V_{REF} + (1/8)V_{REF}$   
 $V_{OUT}(4) = (9/8)V_{REF}$ .
- 6.) Finally, the MSB is 1,  
 switch A is closed, and  
 $V_{OUT}(5) = V_{REF} + (9/16)V_{REF}$   
 $V_{OUT}(5) = (25/16)V_{REF}$ .
- 7.) Finally, the MSB+1 is 0 (always last cycle),  
 switch A is closed, and  
 $V_{OUT}(6) = (25/32)V_{REF}$ .

 **X.6 - CHARACTERIZATION OF ANALOG TO DIGITAL CONVERTERS**General A/D Converter Block DiagramA/D Converter Types




 
- 1.) Serial.
- 2.) Medium speed.
- 3.) High speed and high performance.
- 4.) New converters and techniques.


Characterization of A/D Converters

Ideal Input-Output Characteristics for a 3-bit ADC



  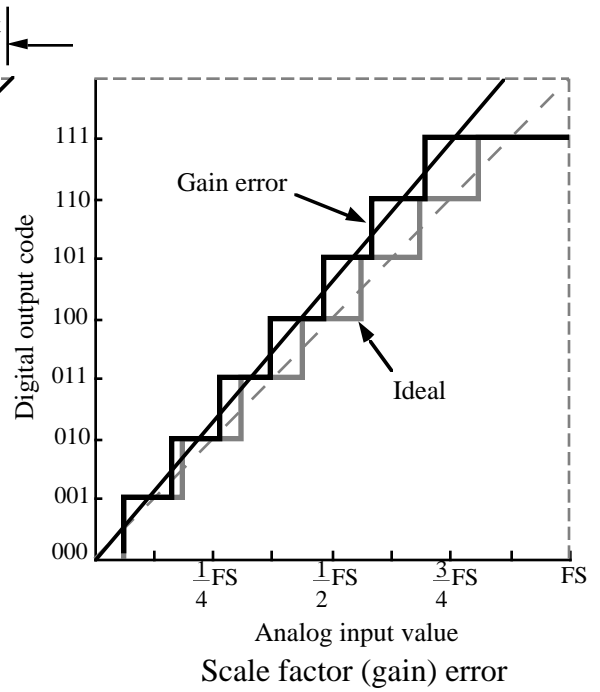 Nonideal Characteristics of A/D Converters



 Sampled Data Aspect of ADC's

$$T_{\text{sample}} = t_s + t_a$$

$t_a$  = acquisition time

$t_s$  = settling time

$t_{\text{ADC}}$  = time for ADC to convert analog input to digital word.


Conversion time =  $t_s + t_a + t_{\text{ADC}}$ .

$$\text{Noise} = \frac{kT}{C} \sqrt{V^2} \text{ (rms)}$$




Sample and Hold Circuits


Simple

 


Improved

 

Waveforms

 


 **X.7 - SERIAL A/D CONVERTERS**Single-Slope, A/D Converter

- Simplicity of operation
- Subject to error in the ramp generator
- Long conversion times

Dual Slope, A/D Converter

Block Diagram:

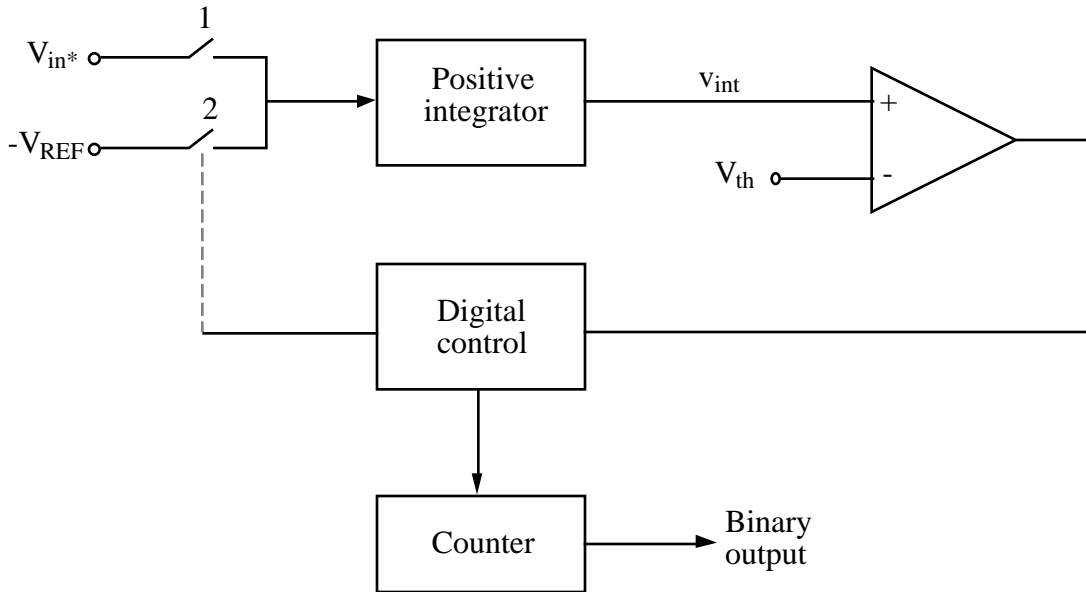

Operation:

- 1.) Initially  $v_{int} = 0$  and  $v_{in}$  is sampled and held ( $V_{in}^* > 0$ ).
- 2.) Reset by integrating until  $v_{int}(0) = V_{th}$ .
- 3.) Integrate  $V_{in}^*$  for  $N_{ref}$  clock cycles to get,


$$v_{int}(t_1) = v_{int}(N_{ref}T) = k \int_0^{N_{ref}T} V_{in}^* dt + v_{int}(0) = kN_{ref}TV_{in}^* + V_{th}$$

- 4.) The Carry Output on the counter is used to switch the integrator from  $V_{in}^*$  to  $-V_{REF}$ . Integrate until  $v_{int}$  is equal to  $V_{th}$  resulting in

$$v_{int}(t_1 + t_2) = v_{int}(t_1) + k \int_{t_1}^{N_{out}T + t_1} -V_{REF} dt = V_{th}$$

$$\therefore kN_{ref}TV_{in}^* + V_{th} - kV_{REF}N_{out}T = V_{th} \Rightarrow \boxed{V_{REF} \frac{N_{out}}{N_{ref}} = V_{in}^*}$$

 
Waveform of the Dual -Slope A/D Converter



- Very accurate method of A/D conversion.
- Requires a long time  $-2(2^N)T$

Switched Capacitor Integrators

Noninverting:

 

Operation:

Assume non-overlapping clocks  $\phi_1$  and  $\phi_2$ . During  $\phi_1$ ,  $C_1$  is charged to  $v_1[(n-1)T]$  giving a charge of  $q_1[(n-1)T]$  on  $C_1$ . During  $\phi_2$ , the charge across  $C_1$  is added to the charge already on  $C_2$  which is  $q_2[(n-1)T]$  resulting in a new charge across  $C_2$  designated as  $q_2(nT)$ . The charge equation can be written as,

$$q_2(nT) = q_2[(n-1)T] + q_1[(n-1)T]$$

or

$$C_2 v_2(nT) = C_2 v_2[(n-1)T] + C_1 v_1[(n-1)T]$$

Using z-domain notation gives

$$C_2 v_2(z) = C_2 z^{-1} v_2(z) + C_1 z^{-1} v_1(z)$$

or

$$H(z) = \frac{v_2(z)}{v_1(z)} = \frac{C_1}{C_2} \left[ \frac{z^{-1}}{1 - z^{-1}} \right]$$

Replacing  $z$  by  $e^{j\omega T}$  gives,

$$H(e^{j\omega T}) = \frac{C_1}{C_2} \left[ \frac{e^{-j\omega T}}{1 - e^{-j\omega T}} \right] = \frac{C_1}{C_2} \left[ \frac{e^{-j\omega \frac{T}{2}}}{e^{j\omega \frac{T}{2}} - e^{-j\omega \frac{T}{2}}} \right]$$

$$= \frac{\omega_0}{j\omega} \underbrace{\left[ \frac{(\omega T/2)}{\sin(\omega T/2)} \right]}_{\text{Mag. error}} \underbrace{\frac{\exp(-j\omega T/2)}{}}_{\text{Phase error}} \approx \frac{\omega_0}{j\omega} \quad \text{if } f \ll f_c = \frac{1}{T}$$


where  $\omega_0 = C_1/(TC_2)$ ,  $\sin x = \frac{e^{jx} - e^{-jx}}{2j}$

Magnitude Plots of the Switched Capacitor Integrator


$$\omega_o = \frac{\omega_c}{2\pi}$$

$$\frac{\omega T}{2} = \frac{2\pi f}{2f_c} = \frac{\pi f}{f_c} = \frac{\pi\omega}{\omega_c}$$

Log Plot-

 


Linear Plot-

 

Switched Capacitor Integrators - Cont'd

Inverting:

 


By a similar analysis, one can show that

$$H(e^{j\omega T}) \approx -\frac{\omega_0}{j\omega}, \text{ if } f \ll f_c = 1/T$$

Settling Time and Slew Rate of the Op Amp

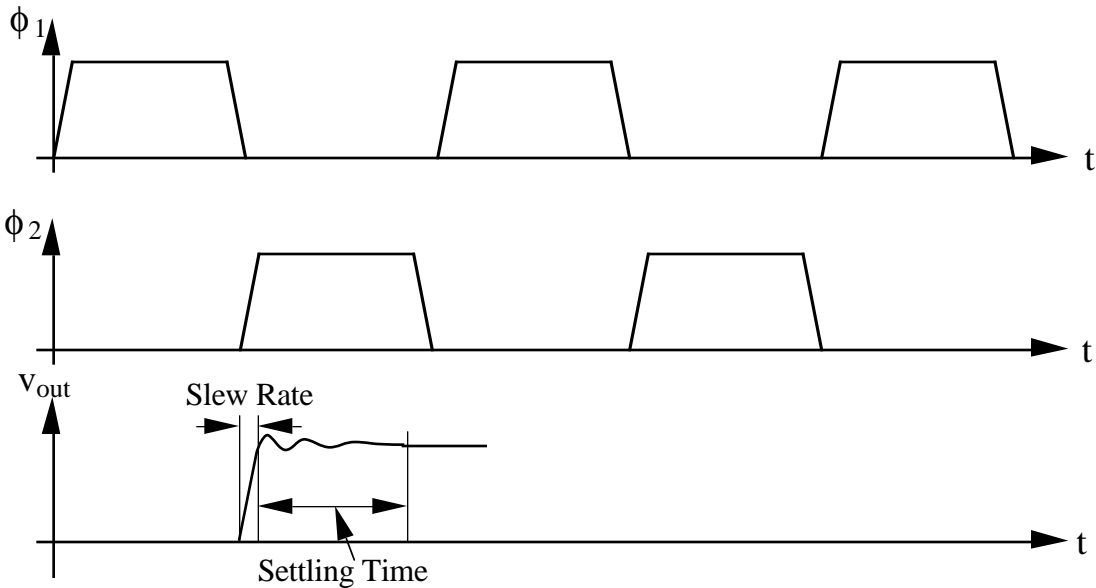Important when the op amp plus feedback circuit has two or more poles or the op amp has a second pole.







**X.8 - MEDIUM SPEED A/D CONVERTERS**


**Conversion Time  $\approx NT$**

Successive Approximation Architecture:

 

Successive Approximation Process:

 


 A Voltage-Charge Scaling Successive Approximation ADC

Operation:

- 1.) With  $S_F$  closed, the bottom plates of all capacitors are connected through switch  $S_B$  to  $V_{in}^*$ . (Automatically accounts for voltage offsets).
- 2.) After  $S_F$  is opened, a successive approximation search among the resistor string taps to find the resistor segment in which the stored sample lies.
- 3.) Buses A and B are then connected across this segment and the capacitor bottom plates are switched in a successive approximation sequence until the comparator input voltage converges back to the threshold voltage.

Capable of 12-bit monotonic conversion with a DL of  $\pm 0.5\text{LSB}$  within  $50\mu\text{s}$ .

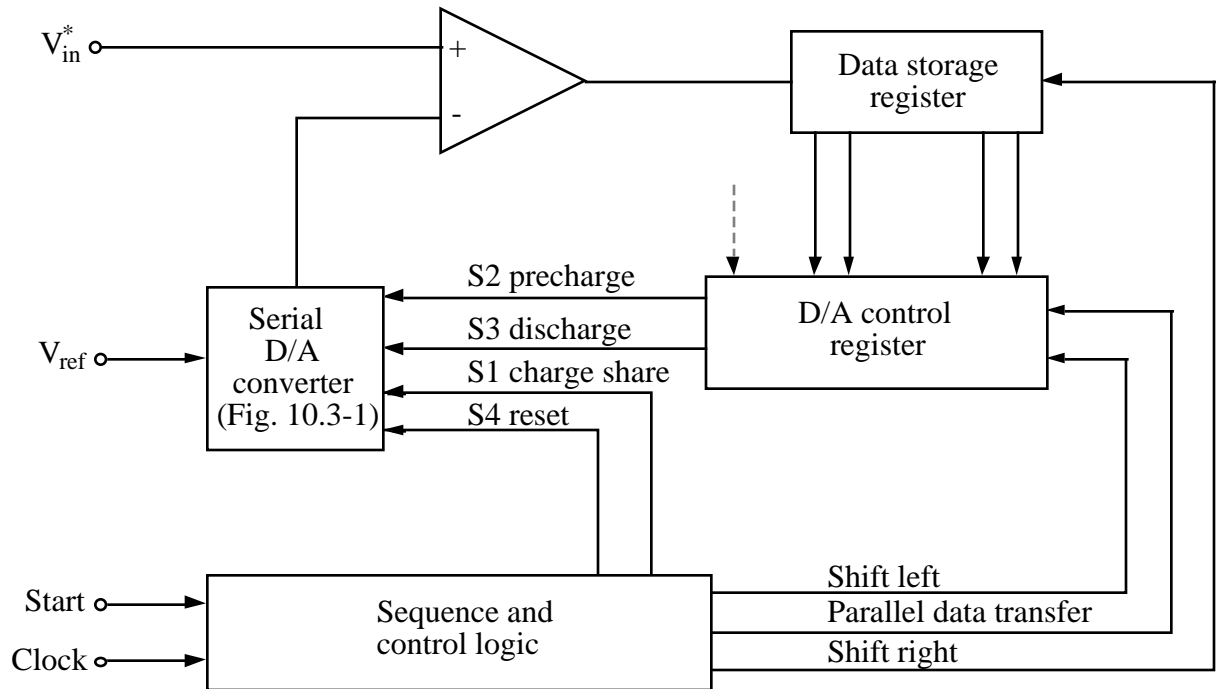A Successive Approximation ADC using a Serial DAC


Conversion Sequence:

- 1.) Assume first  $K$  MSB's have been decided so that,

$$\text{Digital word} = a_M \frac{1}{2^N} + a_{N-1} \frac{1}{2^{N-1}} + \dots + a_{N-K+1} \frac{1}{2^{N-K+1}} + \dots$$

- 2.) Assume  $(K + 1)$ th MSB is 1 and compare this analog output with  $V_{in}^*$  to determine  $a_{N-K}$ .
- 3.) Store  $a_{N-K}$  in the DATA storage register and continue.



**CHARGE REDISTRIBUTION SERIAL DAC**

 

Conversion sequence:

4 Bit D/A Converter

INPUT WORD: 1101

 
 


- Close  $S_4$ :  $V_{C2} = 0$
- Store with LSB first-
- Close  $S_2$  ( $b_0=1$ ):  $V_{C1} = V_{REF}$
- Close  $S_1$ :  $V_{C1} = \frac{V_{REF}}{2} = V_{C2}$
- Close  $S_3$  ( $b_1=0$ ):  $V_{C1} = 0$
- Close  $S_1$ :  $V_{C1} = V_{C2} = \frac{V_{REF}}{4}$
- Close  $S_2$  ( $b_2=1$ ):  $V_{C1} = V_{REF}$
- Close  $S_1$ :  $V_{C1} = V_{C2} = \frac{5}{8} V_{REF}$
- Close  $S_2$  ( $b_3=1$ ):  $V_{C1} = V_{REF}$
- Close  $S_1$ :  $V_{C1} = V_{C2} = \frac{13}{16} V_{REF}$

Comments:

- LSB must go first.
- n cycles to make an n-bit D-A conversion.
- Top plate parasitics add error.
- Switch parasitics add error.

  Serial ADC Waveform for an Input of  $(13/16V_{ref})$




A 1-BIT/PIPE PIPELINE A/D CONVERTER

Single Bit/Stage, N-Stage Pipeline Converter

- Converter in 1 clock cycle using storage registers
- Requires N comparators
- Dependent upon passive component linearity
- Can use error correcting algorithms and self-calibration techniques

 Block Diagram of the 1-Bit/Pipe A/D Architecture



$$V_i = 2V_{i-1} - b_i V_{ref} \quad \text{where} \quad \begin{cases} b_i = +1 & \text{if } V_{i-1} > 0 \\ b_i = -1 & \text{if } V_{i-1} < 0 \end{cases}$$


Output of the n-th stage can be written as:

$$V_N = \prod_{i=1}^N A_i V_{in} - \left[ \sum_{i=1}^{N-1} \left( \prod_{j=i+1}^N A_j \right) b_i + b_N \right] V_{ref}$$


where  $A_j$  and  $b_j$  are the gain and bit value of the  $j$ th stage

Graphical Examples illustrating operation

Example 1

 


Example 2

 

IDEAL STAGE PERFORMANCE

 ith Stage Plot of:  $\frac{V_i}{V_{\text{ref}}} = 2 \frac{V_{i-1}}{V_{\text{ref}}} - b_i$




- 1.)  $b_{i+1}$  must change at 0, and  $\pm 0.5V_{\text{ref}}$ . (when  $V_{i-1}=0$  and  $\pm 0.5V_{\text{ref}}$ )
- 2.)  $b_i$  must change at  $V_i=0$ .
- 3.)  $V_i$  cannot exceed  $V_{\text{ref}}$ .
- 4.)  $V_i$  should not be less than  $V_{\text{ref}}$  when  $V_{i-1}=\pm V_{\text{ref}}$ .





Output Voltage for a 4-stage Converter

 


RESOLUTION LIMITS OF THE 1-BIT/STAGE PIPELINE ADC

1st-Order Errors of The 1-Bit/Stage Pipeline ADC

- Gain magnitude and gain matching ( $k_1$ )
- Offset of the X2 amplifier and the sample/hold ( $k_2$ )
- Comparator offset ( $k_3$ )
- Summer magnitude and gain matching ( $k_4$ )
- Summer offset ( $k_5$ )

Illustration:

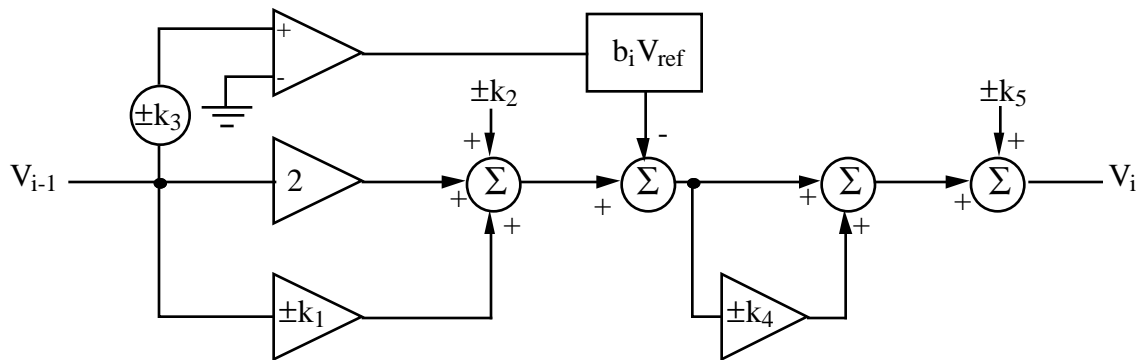

$$V_i = A_i V_{i-1} + V_{OSi} - b_i A_{Si} V_{ref}$$

where 
$$b_i = \begin{cases} +1 & \text{if } V_{i-1} > \pm k_3 = \pm V_{OCi} \\ -1 & \text{if } V_{i-1} < \pm k_3 = \pm V_{OCi} \end{cases}$$

$A_i$  = all gain related errors of the  $i$ th stage

$V_{OSi}$  = system offset errors of the  $i$ th stage

$V_{OCi}$  = the comparator offset of the  $i$ th stage

$A_{Si}$  = the gain of the summing junction of the  $i$ th stage

Generalization of the First-Order Errors

Extending the  $i$ th stage first-order errors to  $N$  stages gives:

$$V_N = \prod_{i=1}^N A_i V_{in} + \left[ \sum_{i=1}^{N-1} \left( \prod_{j=i+1}^N A_j \right) V_{OSi} + V_{OSN} \right] \\ - V_{ref} \left[ \sum_{i=1}^{N-1} \left( \prod_{j=i+1}^N A_j \right) A_{Si} b_i + A_{SN} b_N \right]$$

Assuming identical errors in each stage gives:

$$V_N = A^N V_{in} + \sum_{i=1}^N (A^{N-i}) V_{OS} - V_{ref} \left[ \sum_{i=1}^N (A^{N-i}) A_S b_i \right]$$

Assuming only the first stage has errors:


$$V_N = A_1 2^{N-1} V_{in} + 2^{N-1} V_{OS1} - V_{ref} 2^{N-1} A_{S1} b_1 - V_{ref} \sum_{i=2}^N (2^{N-i}) b_i$$

Identification of Errors

1. Gain Errors

$$\boxed{2^N (\Delta A/A) < 1} \Rightarrow N=10 \Rightarrow \frac{\Delta A}{A} < \frac{1}{1000}$$

Illustration of gain errors

 


Identification of Errors - Cont'd

2. System Offset Errors

$$V_{OS} < \frac{V_{ref}}{2^N}$$

For  $N=10$  and  $V_{ref} = 1V$ ,  $V_{OS} < 1mV$

Illustration of system offset error

 


Identification of Errors - Cont'd
 
## 3. Summing Gain Error

$$\frac{\Delta A_s}{A_s} < \frac{1}{2^N}$$

$$\text{For } N=10, \frac{\Delta A}{A} < \frac{1}{1024}$$



Identification of Errors - Cont'd

## 4. Comparator Offset Error


The comparator offset error is any nonzero value of the input to a stage where the stage bit is caused to change. It can be expressed as:

$$V_i = 2V_{i-1} - b_i V_{\text{ref}}$$

where

$$b_i = \begin{cases} +1 & \text{if } V_{i-1} > V_{\text{OCi}} \\ -1 & \text{if } V_{i-1} < V_{\text{OCi}} \end{cases}$$

Illustration of comparator offset error:

 



## SUMMARY


- 1.) The 1-bit/pipe, pipeline converter which uses standard components including a sample and hold, an amplifier, and a comparator would be capable of realizing at most an 8 or 9 bit converter.
- 2.) The accuracy of the gains and offset of the first stage of an N-Bit converter must be within 0.5LSB.
- 3.) The accuracy of the gains and offset of a stage diminishes with the remaining number of stages to the output of the converter.
- 4.) Error correction and self-calibrating techniques are necessary in order to realize the potential resolution capability of the 1-bit/stage pipeline ADC.

Cyclic Algorithmic A/D Converter


The output of the *i*th stage of a pipeline A/D converter is

$$V_{oi} = (2V_{o,i-1} - b_i V_{REF})z^{-1}$$

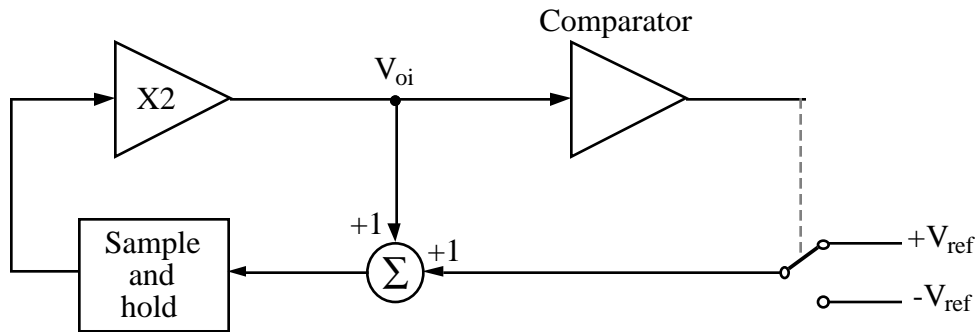If  $V_{oi}$  is stored and feedback to the input, the same stage can be used for the conversion. The configuration is as follows:



Practical implementation:

 



Algorithmic ADC - Example

Assume that  $V_{in}^* = 0.8V_{REF}$ . The conversion proceeds as;

  - 1.)  $0.8V_{REF}$  is sampled and applied to the X2 amplifier by S1.
- 2.)  $V_a(0)$  is  $1.6V_{REF}$  ( $b_1=1$ ) which causes  $-V_{REF}$  to be subtracted from  $V_a(0)$  giving  

$$V_b(0) = 0.6V_{REF}$$
- 3.) In the next cycle,  $V_a(1)$  is  $1.2V_{REF}$  ( $b_2=1$ ) and  $V_b(1)$  is  $0.2V_{REF}$ .
- 4.) The next cycle gives  $V_a(2) = 0.4V_{REF}$  ( $b_3=0$ ) and  $V_b(2)$  is  $0.4V_{REF}$ .
- 5.) The next cycle gives  $V_a(3) = 0.8V_{REF}$  ( $b_4=0$ ) and  $V_b(3)$  is  $0.8V_{REF}$ .
- 6.) Finally,  $V_a(4) = 1.6V_{REF}$  ( $b_5=1$ ) and  $V_b(4) = 0.6V_{REF}$ .

$\therefore$  The digital word is 11001.  $\Rightarrow V_{analog} = 0.78125V_{REF}$ .



Algorithmic A/D Converters-Practical Results

- Only one accurate gain-of-two amplifier required.
- Small area requirements
- Slow conversion time -  $nT$ .
- Errors: Finite op amp gain, input offset voltage, charge injection, capacitance voltage dependence.

Practical Converter


12 Bits

Differential linearity of 0.019% (0.8LSB)

Integral linearity of 0.034% (1.5LSB)

Sample rate of 4KHz.

SELF-CALIBRATING ADC's

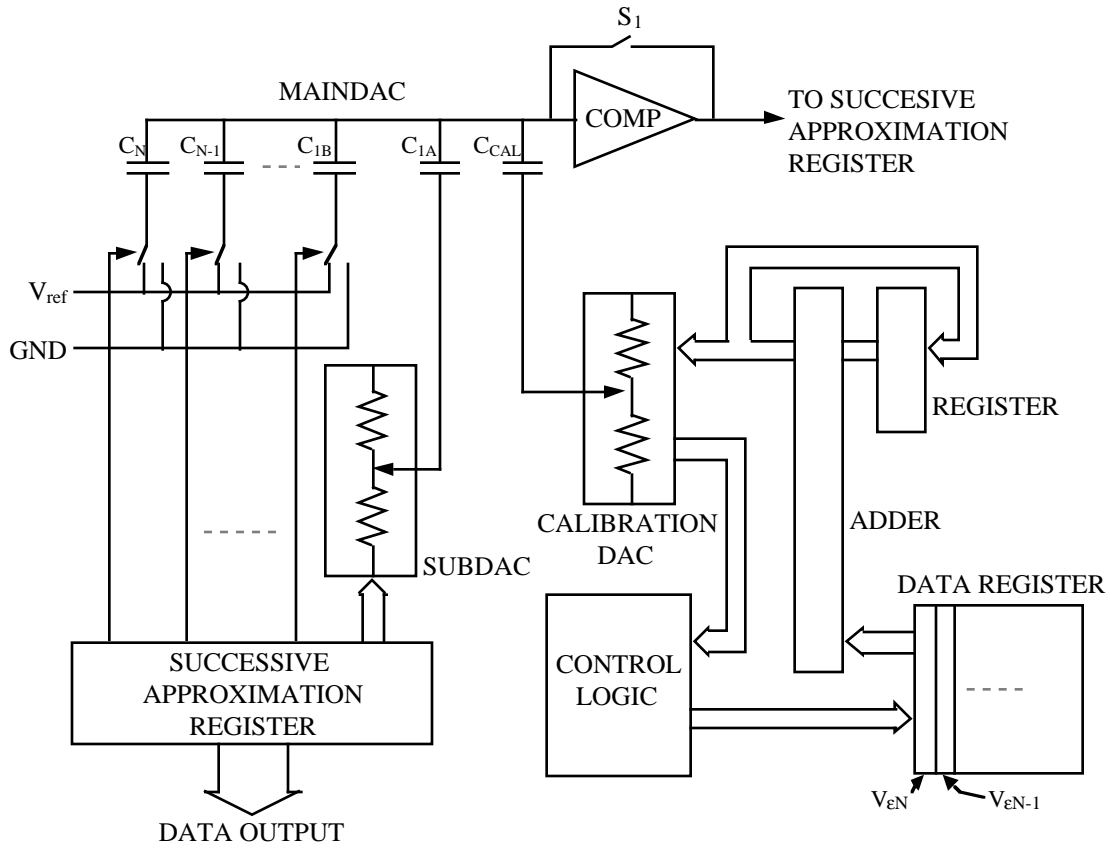

Main ADC is an N-bit charge scaling array.


Sub DAC is an M-bit voltage scaling array.

Calibration DAC is an M+2 bit voltage scaling array.

This is an voltage-scaling, charge-scaling A/D converter with (N+M)- bits resolution.
 
### Self-Calibration Procedure

During calibration cycles, the nonlinearity factors caused by capacitor mismatching are calibrated and stored in the data register for use in the following normal conversion cycles. The calibration procedure begins from MSB by connecting  $C_N$  to  $V_{REF}$  and the remaining capacitors  $C_{NX}$  to GND, then exchange the voltage connection as follows:



where  $C_{NX} = C_{1B} + C_{1A} + \dots + C_{N-1}$

The final voltage  $V_X$  after exchanging the voltage connections is

$$V_X = V_{REF} \frac{C_{NX} - C_N}{C_{NX} + C_N}$$

If the capacitor ratio is accurate and  $C_{NX} = C_N \Rightarrow V_X = 0$ ,

otherwise  $V_X \neq 0$ . This residual voltage  $V_X$  is digitized by the calibration DAC. Other less significant bits are calibrated in the same manner.

After all bits are calibrated, the normal successive-approximation conversion cycles occurs. The calibrated data stored in the data register is converted to an analog signal by calibration DAC and is fed to the main DAC by  $CCAL$  to compensate the capacitor mismatching error.

Self-Calibrating ADC Performance

Supply voltage  $\pm 5V$

Resolution of 16 bits

Linearity of 16 bits

Offset less than 0.25 LSB

Conversion time for 0.5 LSB linearity:

12  $\mu s$  for 12 Bits

80  $\mu s$  for 16 Bits.

RMS noise of 40  $\mu V$ .

Power dissipation of 20 mW (excludes logic)


Area of 7.5 mm (excludes logic).

### **X.9 - HIGH SPEED ADC's**

 **Conversion Time  $\approx T$  (T = clock period)**

- Flash or parallel
- Time interleaving
- Pipeline - Multiple Bits
- Pipeline - Single Bit





FLASH A/D CONVERTER


- Fast conversion time, one clock cycle
- Requires  $2^N - 1$  comparators
- Maximum practical bits is 6 or less
- 6 bits at 10 MHz is practical

Time-Interleaved A/D Converter Array

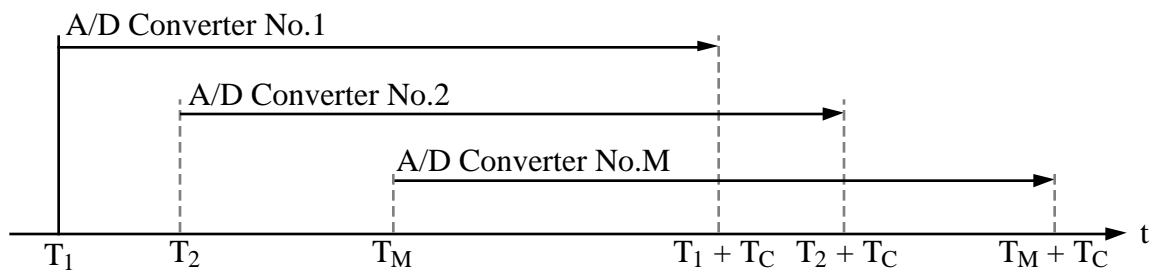 Use medium speed, high bit converters in parallel.




Relative Die Size vs. Number of Bits

 


2M-BIT, PARALLEL-CASCADE ADC

 - Compromise between speed and area
- 8-bit, 1M Hz.



Conversion of Digital back to Analog for Pipeline Architectures

 Use XOR gates to connect to the appropriate point in the resistor divider resulting in the analog output corresponding to the digital output.




## X.10 - OVERSAMPED ( $\Delta$ - $\Sigma$ ) A/D CONVERTER


### NYQUIST VERSUS OVERSAMPLED A/D CONVERTERS

Oversampling A/D converters use a sampling clock frequency( $f_S$ ) much higher than the Nyquist rate( $f_N$ ).

Conventional Nyquist ADC Block Diagram:

 


Oversampling ADC Block Diagram

 

The anti-aliasing filter at the input stage limits the bandwidth of the input signal and prevents the possible aliasing of the following sampling step. The modulator pushes the quantization noise to the higher frequency and leaves only a small fraction of noise energy in the signal band. A digital low pass filter cuts off the high frequency quantization noise. Therefore, the signal to noise ratio is increased.

ANTI-ALIASING FILTER

The anti-aliasing filter of an oversampling ADC requires less effort than that of a conventional ADC. The frequency response of the anti-aliasing filter for the conventional ADC is sharper than the oversampling ADC.

 Conventional ADC's Anti-Aliasing FilterOversampling ADC's Anti-Aliasing Filter

$f_B$  : Signal Bandwidth

$f_N$  : Nyquist Frequency,  $f_N = 2f_B$

$f_S$  : Sampling Frequency and usually  $f_S \gg f_N$


$M$  : Oversampling ratio,  $M = \frac{f_S}{f_N}$

So the analog anti-aliasing filter of an oversampling ADC is less expensive than the conventional ADC. If  $M$  is sufficiently large, the analog anti-aliasing filter is simply an RC filter.

QUANTIZATIONConventional ADC's Quantization

The resolution of conventional ADCs is determined by the relative accuracy of their analog components. For a higher resolution, self-calibration technique can be adopted to enhance the matching accuracy.

Multilevel Quantizer:

 

The quantized signal  $y$  can be represented by  

$$y = Gx + e$$

where,

$G$  = gain of ADC, normally = 1  
 $e$  = quantization error



Conventional ADC's Quantization - Cont'd

The mean square value of quantization error,  $e$ , is

$$e_{\text{rms}}^2 = \frac{1}{\Delta} \int_{-\Delta/2}^{\Delta/2} e(x)^2 dx = \frac{\Delta^2}{12}$$

where

$$\Delta = \text{the quantization level of an ADC (typically } \frac{V_{\text{REF}}}{2^N}\text{)}$$

When a quantized signal is sampled at  $f_S (= 1/\tau)$ , all of its noise power folds into the frequency band from 0 to  $f_S/2$ . If the noise power is white, then the spectral density of the sampled noise is

$$E(f) = e_{\text{rms}} \left( \frac{2}{f_S} \right)^{1/2} = e_{\text{rms}} \sqrt{2\tau}$$

where

$$\tau = 1/f_S \quad \text{and} \quad f_S = \text{sampling frequency}$$


The inband noise energy  $n_o$  is

$$n_o^2 = \int_0^{f_B} E^2(f) df = e_{\text{rms}}^2 (2f_B \tau) = e_{\text{rms}}^2 \left( \frac{2f_B}{f_S} \right) = \frac{e_{\text{rms}}^2}{M}$$

$$n_o = \frac{e_{\text{rms}}}{\sqrt{M}}$$

$$\text{The oversampling ratio } M = \frac{f_S}{2f_B}$$

 Therefore, each doubling of the sampling frequency decreases the in-band noise energy by 3 dB, and increases the resolution by 0.5 bit. This is not a very efficient method of reducing the inband noise.



Oversampling ADCs consist of a  $\Sigma\Delta$  modulator, a decimator (down-sampler), and a digital low pass filter.

### $\Sigma\Delta$ modulator

Also called the noise shaper because it can shape the quantization noise and push majority of the noise to high frequency band. It modulates the analog input signal to a simple digital code, normally is one bit, using a sampling rate much higher the Nyquist rate.

### Decimator



Also called the down-sampler because it down samples the high frequency modulator output into a low frequency output.

### Low-pass filter


Use digital low pass filter to cut off the high frequency quantization noise and preserve the input signal.

Sigma-Delta ( $\Sigma\Delta$ ) ModulatorFirst Order  $\Sigma\Delta$  Modulator

The open loop quantizer in a conventional ADC can be modified by adding a closed loop to become a  $\Sigma\Delta$  modulator.

  Modulator Output

First-Order  $\Sigma\Delta$  Modulator

 

$$y_n = w_n + e_n$$

(1)

$$\begin{aligned} w_{n+1} &= g_n + w_n = x_n - y_n + w_n \\ &= x_n - (w_n + e_n) + w_n = x_n - e_n \end{aligned}$$

(2)


Therefore,  $w_n = x_{n-1} - e_{n-1}$ , which when substituted into (1) gives

$$y_n = x_{n-1} + (e_n - e_{n-1})$$

The output of  $\Sigma\Delta$  modulator  $y_n$  is the input signal delayed by one clock cycle  $x_{n-1}$ , plus the quantization noise difference  $e_n - e_{n-1}$ . The modulation noise spectrum density of  $e_n - e_{n-1}$  is

$$N(f) = E(f) |1 - z^{-1}| = E(f) |1 - e^{-j\omega\tau}| = 2E(f) \sin\left(\frac{\omega\tau}{2}\right) = 2e_{rms} \sqrt{2\tau} \sin\left(\frac{\omega\tau}{2}\right)$$

Plot of Noise Spectrum

 

First Order  $\Sigma\Delta$  Modulator-Cont'd

The noise power in the signal band is

$$n_o^2 = \int_0^{f_B} |N(f)|^2 df = \int_0^{f_B} \left( 2e_{\text{rms}} \sqrt{2\tau} \sin\left(\frac{\omega\tau}{2}\right) \right)^2 df$$

$$n_o^2 = \int_0^{f_B} \left( 2e_{\text{rms}} \sqrt{2\tau} (\pi f\tau) \right)^2 df$$

$$\text{where } \sin\left(\frac{\omega\tau}{2}\right) = \sin\left(\frac{2\pi f}{2f_S}\right) = \sin\left(\frac{\pi f}{f_S}\right) \approx \pi f\tau$$

if  $f_S \gg f$

Therefore,

$$n_o^2 \approx (2\tau)^3 \pi^2 e_{\text{rms}}^2 \int_0^{f_B} f^2 df = \frac{e_{\text{rms}}^2 \pi^2 (2\tau f_B)^3}{3}$$

$$\text{where , } f_S \gg f_B$$

Thus,


$$n_o = e_{\text{rms}} \frac{\pi}{\sqrt{3}} (2f_B\tau)^{3/2} = e_{\text{rms}} \frac{\pi}{\sqrt{3}} M^{-3/2}$$

Each doubling of the oversampling ratio reduces the modulation noise by 9 dB and increase the resolution by 1.5 bits.

Oversampling Ratio Required for a First-Order ΔΣ Modulator

A block diagram for a first-order, sigma-delta modulator is shown in the z-domain. Find the magnitude of the output spectral noise with  $V_{IN}(z) = 0$  and determine the bandwidth of a 10-bit analog-to-digital converter if the sampling frequency,  $f_S$ , is 10 MHz.

Solution

 

$V_{out}(z) = e_{rms} + \left(\frac{1}{z-1}\right) [V_{in}(z) - V_{out}(z)]$   
or

$$V_{out}(z) = \left(\frac{z-1}{z}\right) e_{rms} \text{ if } V_{in}(z) = 0 \rightarrow V_{out}(z) = (1-z^{-1})e_{rms}$$

$$|N(f)| = E(f) |1 - e^{-j\omega\tau}| = 2E(f) \sin\left(\frac{\omega\tau}{2}\right) = 2\sqrt{\frac{2}{f_S}} e_{rms} \sin\left(\frac{\omega\tau}{2}\right)$$

The noise power is found as

$$n_o^2(f) = \int_0^{f_B} |N(f)|^2 df = \int_0^{f_B} \left(2\sqrt{\frac{2}{f_S}} e_{rms}\right)^2 \sin^2\left(\frac{2\pi f\tau}{2}\right) df$$

Let  $\sin\left(\frac{2\pi f\tau}{2}\right) \approx \pi f\tau$  if  $f_S \gg f_B$ . Therefore,

$$n_o^2(f) = 4\left(\frac{2}{f_S}\right) e_{rms}^2 (\pi\tau)^2 \int_0^{f_B} f^2 df = \frac{8\pi^2}{3} e_{rms}^2 \left(\frac{f_B}{f_S}\right)^3$$

or

$$n_o(f) = \sqrt{\frac{8}{3}} \pi \cdot e_{rms} \left(\frac{f_B}{f_S}\right)^{3/2} \leq \frac{V_{REF}}{2^{10}}$$



Solving for  $f_B/f_S$  gives (using  $\Delta$  in  $e_{rms}$  term is equal to  $V_{REF}$ )

$$\frac{f_B}{f_S} = \left[ \left( \frac{\sqrt{12}\sqrt{3}}{\sqrt{8}\pi} \right) \frac{1}{2^{10}} \right]^{2/3} = [0.659 \times 10^{-3}]^{2/3} = 0.007576$$

$$f_B = 0.007576 \cdot 10\text{MHz} = 75.76\text{kHz}.$$

Decimator (down-sampling)

 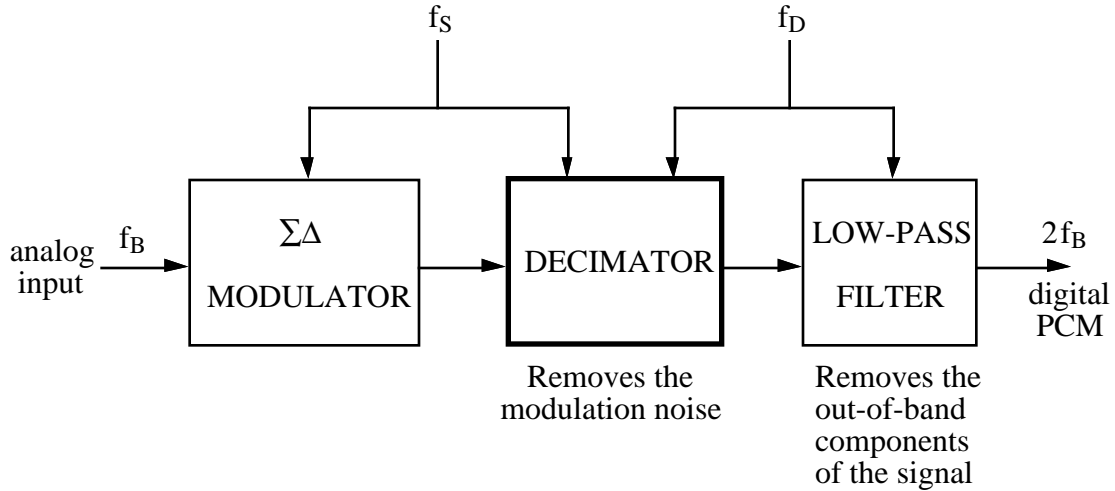The one-bit output from the  $\Sigma\Delta$  modulator is at very high frequency, so we need a decimator (or down sampler) to reduce the frequency before going to the digital filter.



$$y_n = \frac{1}{N} \sum_{N=0}^N x_n, \text{ where } N = \frac{f_S}{f_D} = \text{down-sampling ratio}$$


The transfer function of decimator is

$$H(z) = \frac{Y(z)}{X(z)} = \frac{1}{N} \sum_{i=0}^{N-1} z^{-i} = \frac{1}{N} \frac{1 - z^{-N}}{1 - z^{-1}}$$

$$H(e^{j\omega\tau}) = \frac{\text{sinc}(\pi f N \tau)}{\text{sinc}(\pi f \tau)}$$

Frequency Spectrum of the Decimator

 
$$H(e^{j\omega\tau}) = \frac{\text{sinc}(\pi f N \tau)}{\text{sinc}(\pi f \tau)}$$




$f_D$  = intermediate decimation frequency

 
When the modulation noise is sampled at  $f_D$ , its components in the vicinity of  $f_D$  and the harmonics of  $f_D$  fold into the signal band. Therefore, the zeros of the decimation filter must be placed at these frequencies.



Digital Lowpass Filter

FIR or IIR digital low pass filter

 

 After Digital Low Pass FilteringBit resolution


From the frequency response of above diagram, the signal-to-noise ratio (SNR)

$$\text{SNR} = 10 \log_{10} \frac{\text{signal}}{f_B \sum_{f=0} \text{noise}(f)} \quad (\text{dB})$$

and


$$\text{Bit resolution (B)} \approx \frac{\text{SNR}(\text{db})}{6\text{dB}}$$

 System block in time domain and frequency domain



Second-Order  $\Sigma\Delta$  Modulator

 Second order  $\Sigma\Delta$  modulator can be implemented by cascading two first order  $\Sigma\Delta$  modulators.




$$y_n = x_{n-1} + (e_n - 2e_{n-1} + e_{n-2})$$

The output of a second order  $\Sigma\Delta$  modulator  $y_n$  is the input signal delayed by one clock cycle  $x_{n-1}$ , plus the quantization noise difference  $e_n - 2e_{n-1} + e_{n-2}$ . The modulation noise spectrum density of  $e_n - 2e_{n-1} + e_{n-2}$  is

$$N(f) = E(f) \left| 1 - z^{-1} \right|^2 = E(f) \left| 1 - e^{-j\omega\tau} \right|^2 = 4E(f) \sin^2\left(\frac{\omega\tau}{2}\right)$$

Noise Spectrum

 

Second-Order  $\Sigma\Delta$  Modulator- Cond'd

The noise power in the signal band is

$$n_o = e_{\text{rms}} \frac{\pi^2}{\sqrt{5}} M^{-5/2} = \sqrt{\frac{\Delta^2}{12}} \frac{\pi^2}{\sqrt{5}} M^{-5/2} = \frac{\Delta\pi}{2\sqrt{15}} (M)^{-5/2}, f_s \gg f_o$$

Each doubling of the oversampling ratio reduces the modulation noise by 15 dB and increase the resolution by 2.5 bits.

Higher-Order  $\Sigma-\Delta$  Modulators

Let  $L$  = the number of loops. The spectral density of the modulation can be written as

$$|N_L(f)| = e_{\text{rms}} \sqrt{2\tau} \left[ 2\sin\left(\frac{\omega\tau}{2}\right) \right]^L$$

The rms noise in the signal band is given approximately by

$$n_o \approx e_{\text{rms}} \frac{\pi^L}{\sqrt{2L+1}} (2f_B\tau)^{L+0.5}$$

This noise falls  $3(2L+1)$  dB for every doubling of the sampling rate providing  $L+0.5$  extra bits.

Decimation Filter

A filter function of  $\left[ \frac{\text{sinc}(\pi f N \tau)}{\text{sinc}(\pi f \tau)} \right]^{L+1}$  is close to being optimum for decimating the

signal from an  $L$ th-order  $\Delta-\Sigma$  modulator.


Stability

For orders greater than 2, the loop can become unstable. Loop configuration must be used that provide stability for order greater than two.

The modulation noise spectral density of a second-order, 1-bit  $\Delta\Sigma$  modulator is given as

$$|N(f)| = \frac{4\Delta}{\sqrt{12}} \sqrt{\frac{2}{f_s}} \sin^2\left(\frac{\omega t}{4}\right)$$

where  $\Delta$  is the signal level out of the 1-bit quantizer and  $f_s = (1/\tau) =$  the sampling frequency and is 10MHz. Find the signal bandwidth,  $f_B$ , in Hz if the modulator is to be used in an 18 bit oversampled ADC. Be sure to state any assumption you use in working this problem.

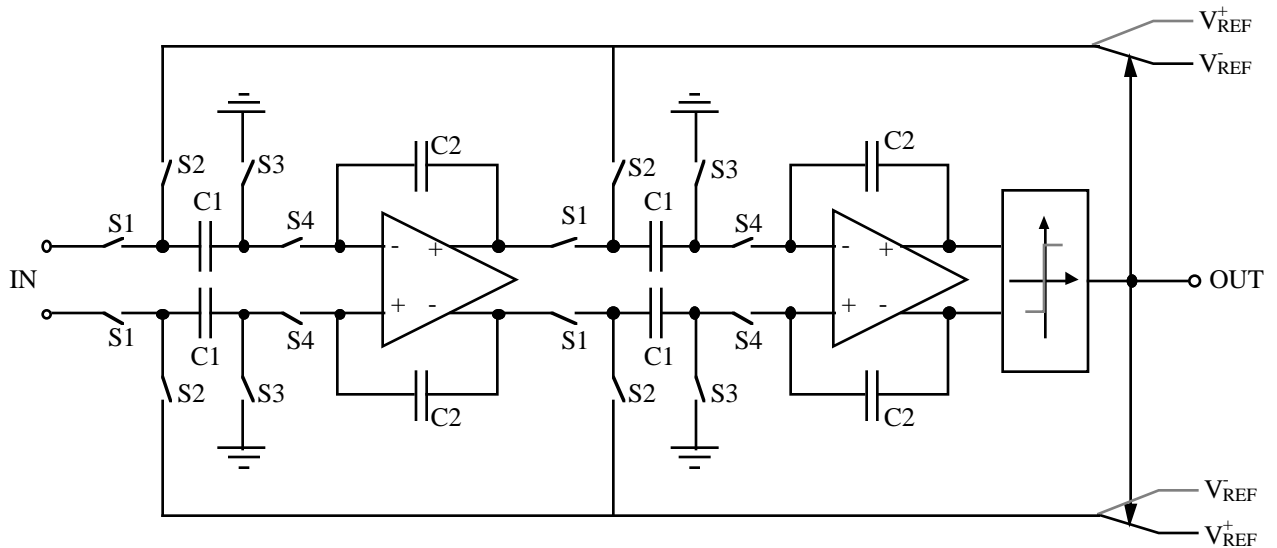Circuit Implementation of A Second Order  $\Sigma\Delta$  Modulator

Fully differential, switched-capacitor integrators can reduce charge injection effect.

Circuit Tolerance of a Second Order  $\Sigma\Delta$  Modulator

1. 20% variation of  $C1/C2$  has only a minor impact on performance.
2. The Op Amp gain should be comparable to the oversampling ratio.
3. The unity-gain bandwidth of Op Amp should be at least an order of magnitude greater than the sampling rate.

SOURCES OF ERRORS IN  $\Sigma\Delta$  A/D CONVERTERS

1. Quantization in time and amplitude

Jitter and hysteresis

2. Linear Errors

Gain and delay

3. Nonlinear Errors

Harmonic distortion

Thermal noise



Comparison of the Various Examples Discussed

Type of Converter	No. of Cycles/Conversion	No. of Comparators	Dependent on Passive Components	Resolution	Speed	INL/DNL (LSB's)	Area	Power (mW)
Flash	1	$2^N-1$	Yes	Low	High	N/A	Largest	Largest
Two-Step Flash	2	31	Yes	10 bits	5Ms/s	$\pm 3/\pm 0.6$	54k mils <sup>2</sup>	350
Pipeline	1 after initial delay	3	Yes	13 bits	250ks/s	$\pm 1.5/\pm 0.5$	3600 mils <sup>2</sup>	15
Oversampling	64	3	Yes	16 bits	24kHz	91dB	75.3k mils <sup>2</sup>	110

## **X.11 -FUNDAMENTAL LIMITS OF SAMPLING A/D CONVERTERS**

### kT/C Noise

Assume that the ON resistance of a switch is R and the sampling capacitor is C and that the time to charge the capacitor fully is

$$T = \frac{1}{f_c} \approx 10RC \quad (1)$$

Set the value of the LSB  $\left( = \frac{V_{\text{ref}}}{2^N} \right)$  equal to kT/C noise of the switch,

$$\frac{V_{\text{ref}}}{2^N} = \sqrt{\frac{kT}{C}} \quad (2)$$

Solve for C of (1) and substitute into (2) to get

$$\left( \frac{V_{\text{ref}}}{2^N} \right)^2 = 10kTRf_c \Rightarrow 2^N \sqrt{f_c} = \frac{V_{\text{ref}}}{\sqrt{10kRT}} \quad (3)$$

Taking the log of both sides of (3) gives

$$N = -1.67 \log(f_c) + 3.3 \log(V_{\text{ref}}) - 1.67 \log(10kRT)$$

or

$$\boxed{N = 32.2 + 3.33 \log(V_{\text{ref}}) - 1.67 \log(Rf_c)}$$

(At room temperature)

### kT/C Noise

Comparison of high-performance, monolithic A/D converters in terms of resolution versus sampling frequency with fundamental limits due to kT/C noise superimposed.

## Fundamental Limits of Sampling A/D Converters - Continued

### Maximum Sample Rate


Assume that the maximum sample rate is determined by the time required for the amplifiers and/or sample-hold circuits to settle with the desired accuracy for high resolution. Further assume that the dynamics of these circuits can be modeled by a second-order system with a transfer function of

$$\frac{A(s)}{A(0)} = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

If  $\omega_n \approx \text{GB}$  of the circuit and if the system is underdamped, then the step response is given as

$$\frac{v_o(t)}{A(0)} = 1 - \left[ \frac{e^{-\zeta\text{GB}t}}{\sqrt{1-\zeta^2}} \right] \sin(\sqrt{1-\zeta^2} \text{GB} \cdot t + \phi)$$

This response looks like the following,

 

If we define the error ( $\pm\epsilon$ ) in  $v_o$  settling to  $A(0)$  as the multiplier of the sinusoid, then an expression for the settling time can be derived as


$$t_s = \frac{1}{2\pi\zeta\text{GB}} \ln\left(\frac{e^{-\zeta\text{GB}t}}{\sqrt{1-\zeta^2}}\right) \Rightarrow f_{\text{sample}} = \frac{1}{t_s} = \frac{2\pi\zeta\text{GB}}{\ln\left(\frac{1}{\epsilon\sqrt{1-\zeta^2}}\right)}$$

For reasonable values of  $\zeta$ ,  $f_{\text{sample}}$  can be approximated as

$$\boxed{f_{\text{sample}} \approx \frac{\pi\text{GB}}{10} = \frac{\text{GB}}{3}}$$

Aperature Uncertainty (Jitter)

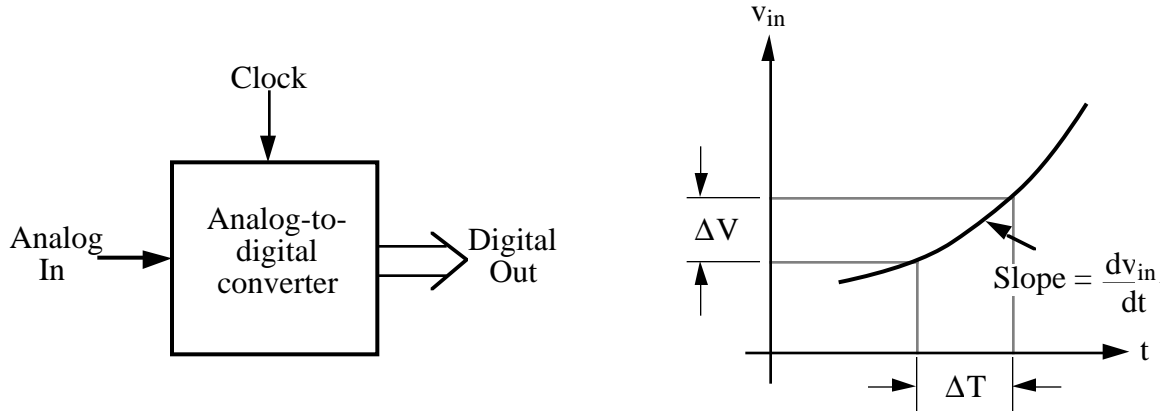A problem in all clocked or sampled A/D converters.



$$\Delta V = \text{slope} \times \Delta T = \frac{dv_{in}}{dt} \Delta T$$

$$\Delta T = \text{Aperature uncertainty} = \frac{\Delta V}{\frac{dV_{in}}{dt}} = \frac{V_{ref}/2^N}{dv_{in}/dt}$$

Assume that  $v_{in}(t) = V_p \sin \omega t$

$$\left| \frac{dv_{in}}{dt} \right|_{\max} = \omega V_p$$

$$\Delta T = \frac{V_{ref}}{2^N} \times \frac{1}{\omega V_p} \approx \frac{V_{ref}}{2^N \omega V_{ref}} = \frac{1}{2^N \omega}$$

Therefore,  $\Delta T = \frac{1}{2\pi f 2^N} = \frac{1}{\pi f 2^{N+1}}$

Suppose  $f = 100\text{kHz}$  and  $N = 8$ ,  $\Delta T = \frac{1}{200\pi \text{K} \times 2^9} = 6.22\text{ns}$

Clock accuracy =  $\frac{6.22\text{ns}}{10,000\text{ns}} = 0.06\% = \frac{622\text{ppm}}{?}$

## **X.12 - SUMMARY OF A/D CONVERTERS**

### Typical Performance Characteristics

A/D Architecture	Typical Performance Characteristics
Serial $\frac{1}{f_c} = 2NT$	1-100 conversions/sec., 12-14 bit accuracy, requires no element-matching, a stable voltage reference is necessary
Successive Approximation $\frac{1}{f_c} \approx NT$	10,000-100,000 conversions/sec., 8-10 bits of untrimmed or uncalibrated accuracy, 12-14 bits of trimmed or calibrated accuracy
High Speed $T < \frac{1}{f_c} < NT$	1 to 40 megaconversions/sec., 7-9 bits of accuracy, 10-12 bits of accuracy with error correction and other techniques
Oversampling $\frac{1}{f_c} \ll T$	8,000-600,000 conversions/sec., 12-16 bits accuracy, requires linear integrators but no precision passive components, minimizes noise and offsets

### Conclusions

- The best A/D converter depends upon the application
- Both resolution and speed are ultimately limited by the accuracy of the process
- High resolution A/D's will be more oriented toward "signal averaging" type converters, particularly with shorter channel lengths